

Operating Signal by Amplifier

Sung Han Ro

KAIST

Physical Mathematics I Conference
12 December 2009

Structure of Operating Signal

Operating signal is essential technique of modern computing system. Nice signal and operating signals are required to have several properties.

Structure of Operating Signal

Operating signal is essential technique of modern computing system. Nice signal and operating signals are required to have several properties.

- First of all, What is Signal?

Structure of Operating Signal

Operating signal is essential technique of modern computing system. Nice signal and operating signals are required to have several properties.

- First of all, What is Signal?
 - Signal is any time varying or spatial varying quantity
 - Signal can carry information

Structure of Operating Signal

Operating signal is essential technique of modern computing system. Nice signal and operating signals are required to have several properties.

- First of all, What is Signal?
 - Signal is any time varying or spatial varying quantity
 - Signal can carry information
- Which quantity is good for Signal?

Structure of Operating Signal

Operating signal is essential technique of modern computing system. Nice signal and operating signals are required to have several properties.

- First of all, What is Signal?
 - Signal is any time varying or spatial varying quantity
 - Signal can carry information
- Which quantity is good for Signal?
Voltage!

Structure of Operating Signal

Operating signal is essential technique of modern computing system. Nice signal and operating signals are required to have several properties.

- First of all, What is Signal?
 - Signal is any time varying or spatial varying quantity
 - Signal can carry information
- Which quantity is good for Signal?
Voltage!
- Signal Operation

Objects used in operation

Resistor



Diode



Capacitor



Coil



Transformer



- Resistor

$$I = \frac{V}{R} \quad (1)$$

- Diode

$$I = I_0 e^{kV} \quad (2)$$

- Capacitor

$$I = C \frac{d}{dt} V \quad (3)$$

- Coil

$$I = -\frac{1}{L} \int V dt \quad (4)$$

- Transformer

$$V_{out} = \frac{N_{in}}{N_{out}} V_{in} \quad (5)$$

Objects used in operation

Resistor



Diode



Capacitor



Coil



Transformer



- Resistor

$$I = \frac{V}{R} \quad (1)$$

- Diode

$$I = I_0 e^{kV} \quad (2)$$

- Capacitor

$$I = C \frac{d}{dt} V \quad (3)$$

- Coil

$$I = -\frac{1}{L} \int V dt \quad (4)$$

- Transformer

$$V_{out} = \frac{N_{in}}{N_{out}} V_{in} \quad (5)$$

Structure of Operating Signal

Operating signal is essential technique of modern computing system. Nice signal and operating signals are required to have several properties.

- First of all, What is Signal?
 - Signal is any time varying or spatial varying quantity
 - Signal can carry information
- Which quantity is good for Signal?
Voltage!
- Signal Operation

Structure of Operating Signal

Operating signal is essential technique of modern computing system. Nice signal and operating signals are required to have several properties.

- First of all, What is Signal?
 - Signal is any time varying or spatial varying quantity
 - Signal can carry information
- Which quantity is good for Signal?
Voltage!
- Signal Operation
 - Input and output signal have to be same type
 - Operating method should cover general cases

Structure of Operating Signal


Operating signal is essential technique of modern computing system. Nice signal and operating signals are required to have several properties.

- First of all, What is Signal?
 - Signal is any time varying or spatial varying quantity
 - Signal can carry information
- Which quantity is good for Signal?
Voltage!
- Signal Operation
 - Input and output signal have to be same type
 - Operating method should cover general cases

How??


Operational amplifier

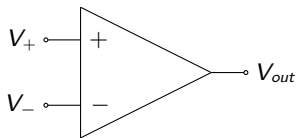As a base of signal operation, Operational amplifier is widely used




Operational amplifier

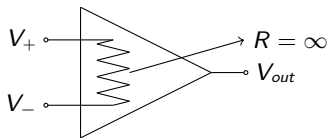As a base of signal operation, Operational amplifier is widely used



Operational amplifier

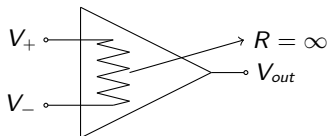
As a base of signal operation, Operational amplifier is widely used



$$V_{out} = \lim_{G \rightarrow \infty} G (V_+ - V_-) \quad (6)$$

Operational amplifier

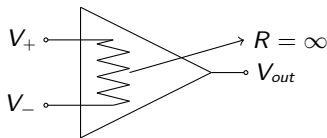
As a base of signal operation, Operational amplifier is widely used




$$V_{out} = \lim_{G \rightarrow \infty} G (V_+ - V_-) \quad (6)$$

- OP-amp amplify input voltage with Gain G
- In ideal case, G is infinitely large number

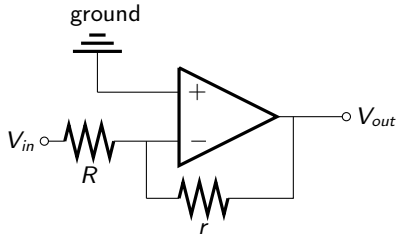Simple OP-amp circuit : Inverting amplifier




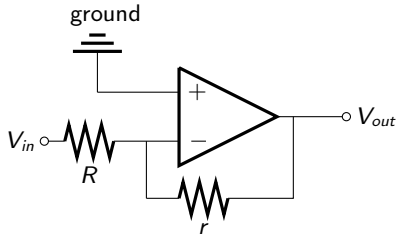Simple OP-amp circuit : Inverting amplifier




- V_{out} and V_- connected

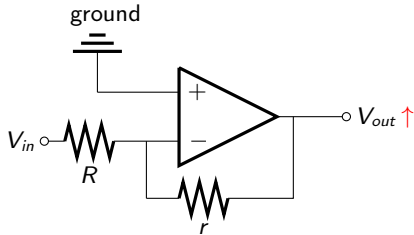Simple OP-amp circuit : Inverting amplifier




- V_{out} and V_- connected

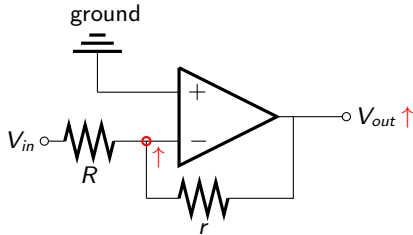Simple OP-amp circuit : Inverting amplifier




- V_{out} and V_- connected

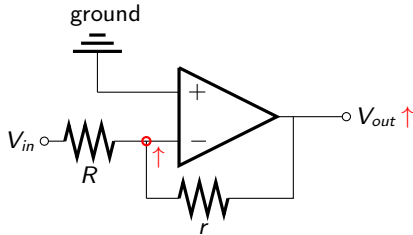Simple OP-amp circuit : Inverting amplifier



- V_{out} and V_- connected
 - $V_{out} \rightarrow$ Finite

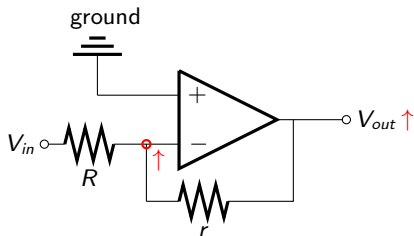
Simple OP-amp circuit : Inverting amplifier



- V_{out} and V_- connected


- $V_{out} \rightarrow \text{Finite}$
- Finite $V_{out} \rightarrow V_- = V_+ = 0$ [Remind $\lim_{G \rightarrow \infty} G(V_+ - V_-)$]

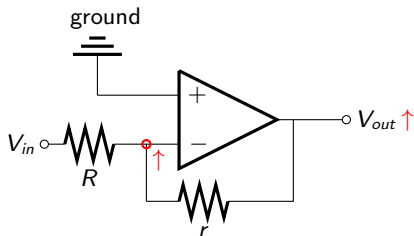Simple OP-amp circuit : Inverting amplifier



- V_{out} and V_- connected
 - $V_{out} \rightarrow \text{Finite}$
 - Finite $V_{out} \rightarrow V_- = V_+ = 0$
- $V_{in} \rightarrow V_{out}$ current
 - $i = V_{in}/R = -V_{out}/r$

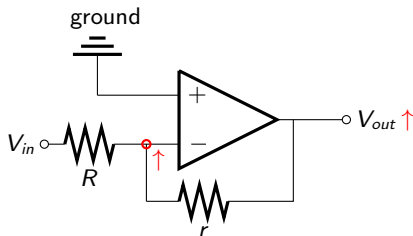
Simple OP-amp circuit : Inverting amplifier




- V_{out} and V_- connected
 - $V_{out} \rightarrow \text{Finite}$
 - Finite $V_{out} \rightarrow V_- = V_+ = 0$
- $V_{in} \rightarrow V_{out}$ current
 - $i = V_{in}/R = -V_{out}/r$

$$V_{out} = -\frac{r}{R} V_{in} \quad (7)$$


Principle of OP-amp operation

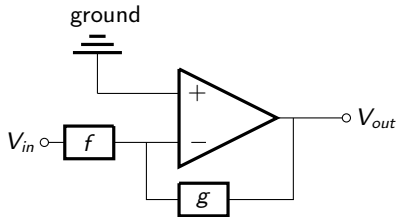


Principle of OP-amp operation

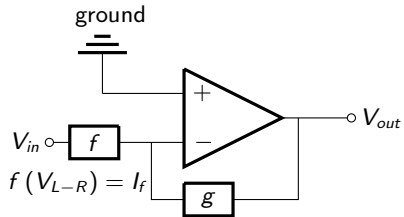

Principle of OP-amp operation

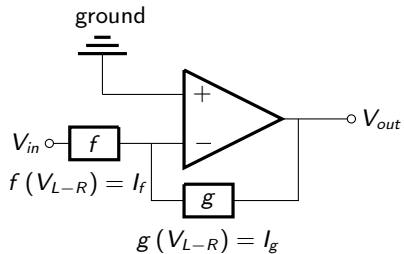


Principle of OP-amp operation

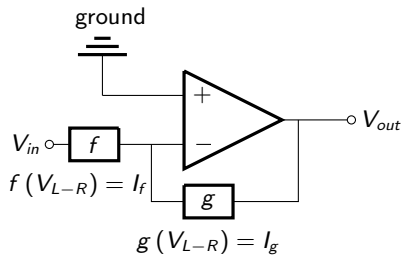

- **Negative feedback**

- V_{out} fixed on equilibrium value
- Finite $V_{out} \rightarrow V_- = V_+ = 0$


Principle of OP-amp operation

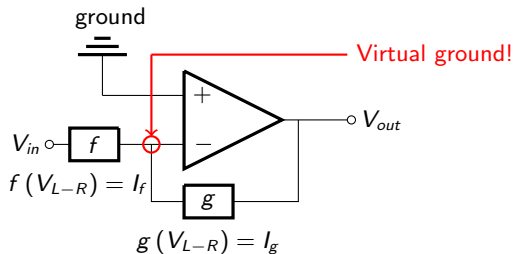

- Negative feedback


- V_{out} fixed on equilibrium value
- Finite $V_{out} \rightarrow V_- = V_+ = 0$

Principle of OP-amp operation

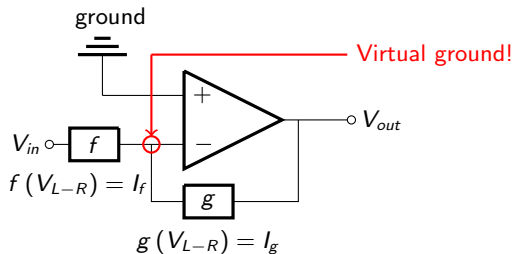


- Negative feedback
 - V_{out} fixed on equilibrium value
 - Finite $V_{out} \rightarrow V_- = V_+ = 0$
- $V \rightarrow I \rightarrow V$

Principle of OP-amp operation

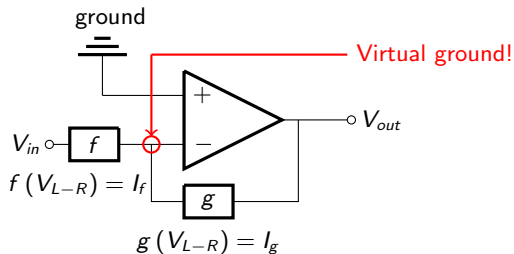

- Negative feedback
 - V_{out} fixed on equilibrium value
 - Finite $V_{out} \rightarrow V_- = V_+ = 0$
- $V \rightarrow I \rightarrow V$
 - Current fixed at $I_{in} = f(V_{in})$

Principle of OP-amp operation

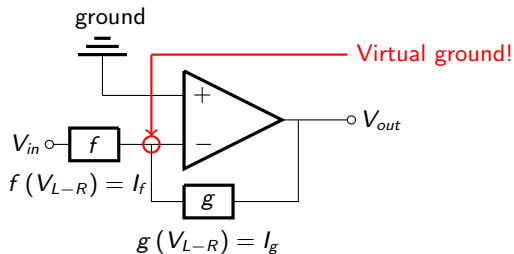


- Negative feedback

- V_{out} fixed on equilibrium value
- Finite $V_{out} \rightarrow V_- = V_+ = 0$

- $V \rightarrow I \rightarrow V$

- Current fixed at $I_{in} = f(V_{in})$
- Current also satisfy $I_{in} = g(-V_{out})$

Principle of OP-amp operation

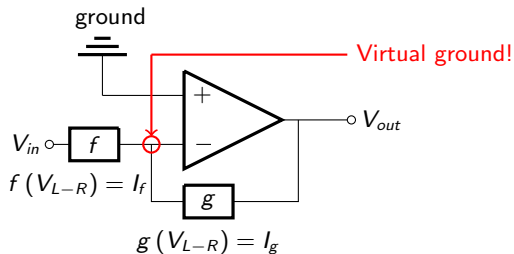

- Negative feedback


- V_{out} fixed on equilibrium value
- Finite $V_{out} \rightarrow V_- = V_+ = 0$

- $V \rightarrow I \rightarrow V$


- Current fixed at $I_{in} = f(V_{in})$
- Current also satisfy $I_{in} = g(-V_{out})$

$$V_{out} = -g^{-1}[f(V_{in})] \quad (8)$$


Exponential operator

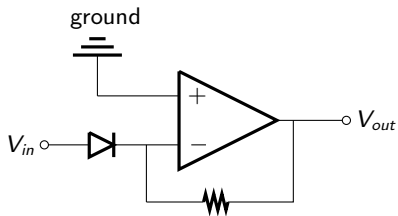


Exponential operator

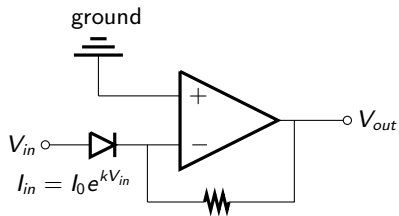


Exponential operator

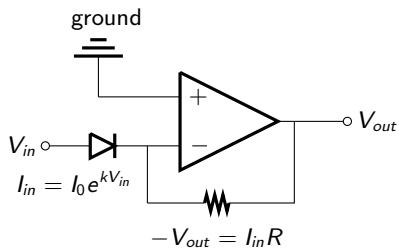


Exponential operator

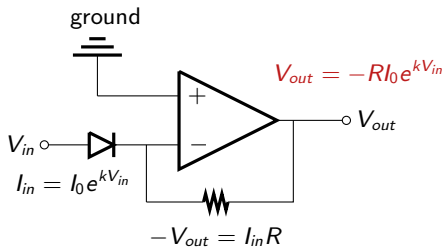


Exponential operator

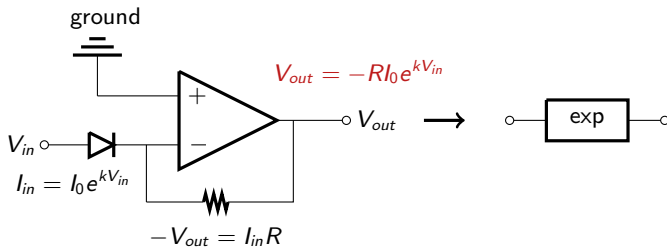


Logarithmic operator

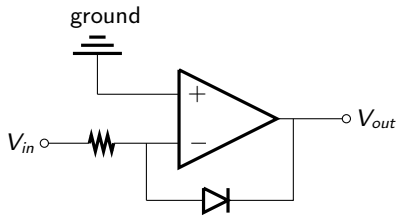


Logarithmic operator

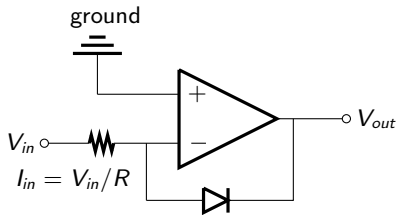


Logarithmic operator

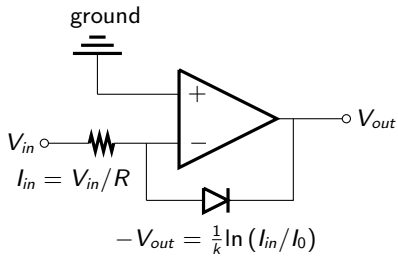


Logarithmic operator

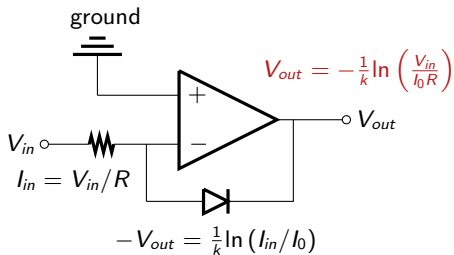


Logarithmic operator

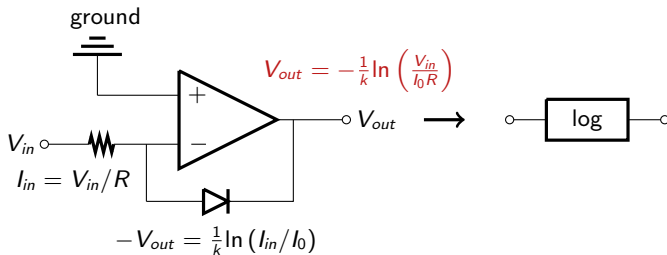


Differential operator

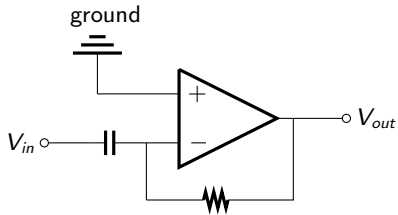


Differential operator

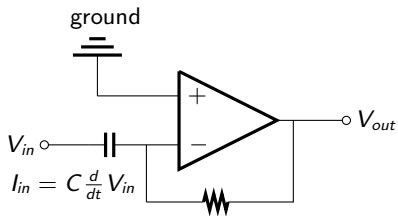


Differential operator

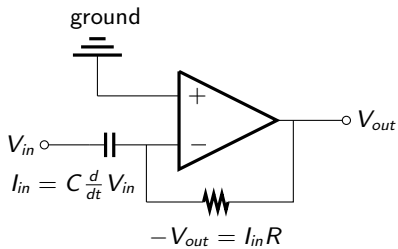


Differential operator

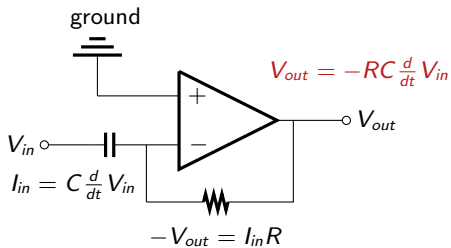


Differential operator

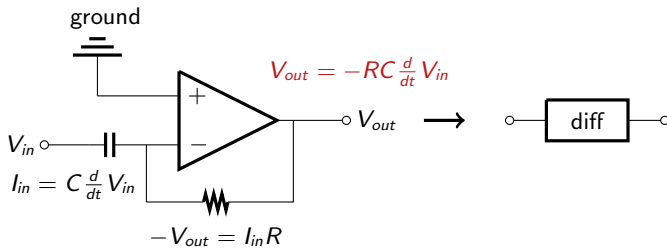


Integral operator

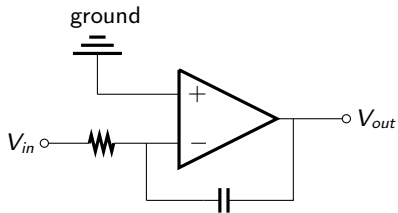


Integral operator

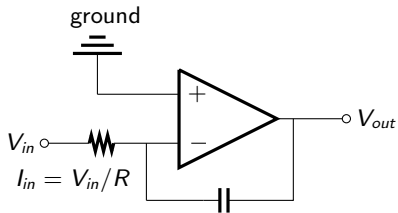


Integral operator

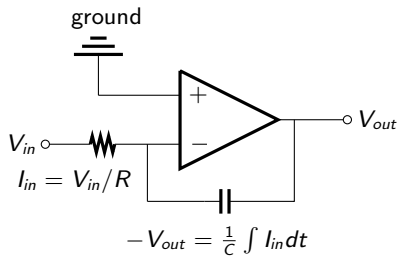


Integral operator

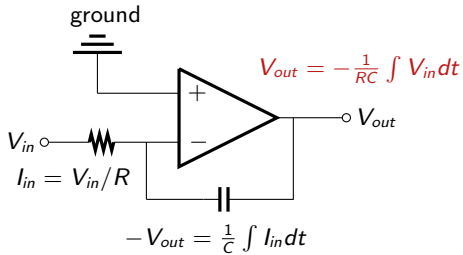


Integral operator

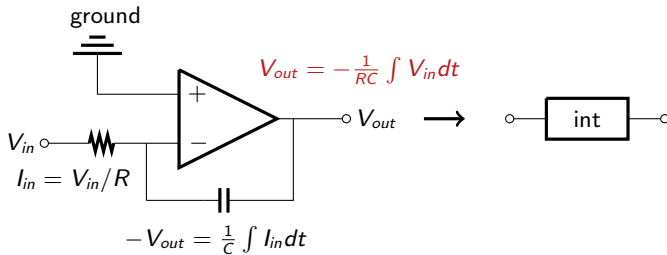


Addition operator

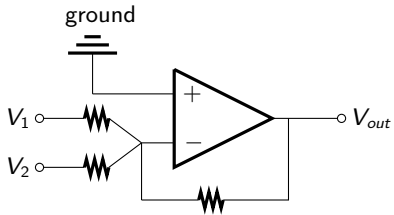


Addition operator

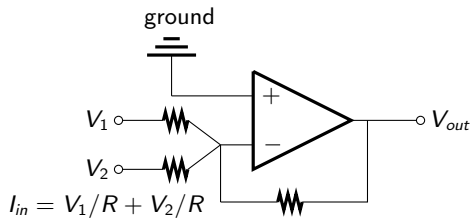


Addition operator

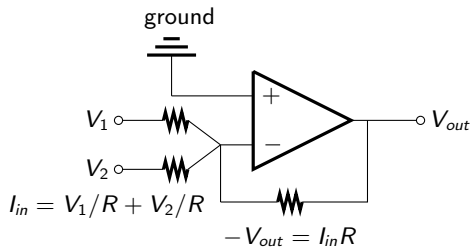

Addition operator

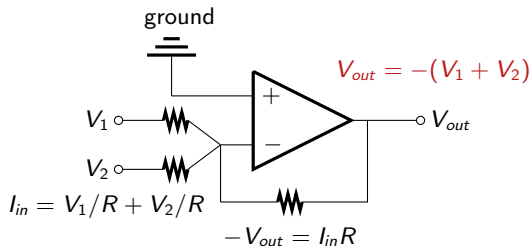


Addition operator

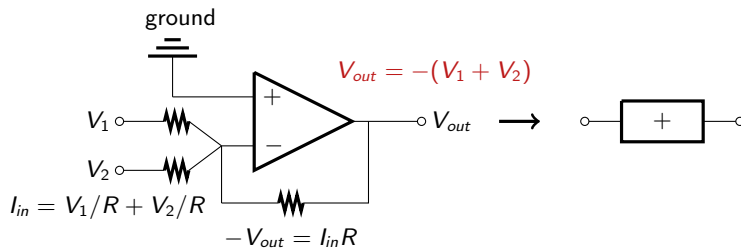


Multiplication operator


Multiplication operator

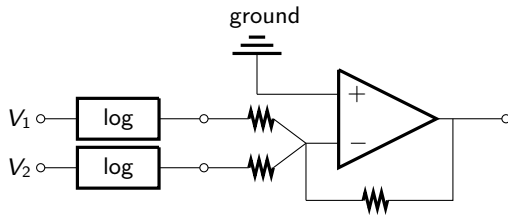


Multiplication operator

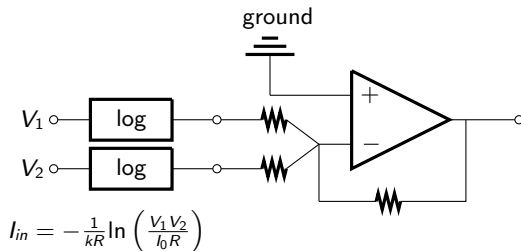


Multiplication operator

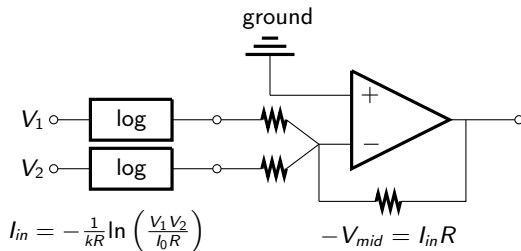


Multiplication operator

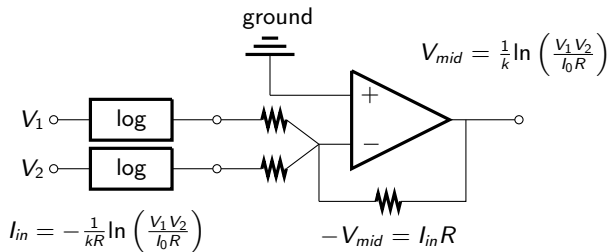

Multiplication operator

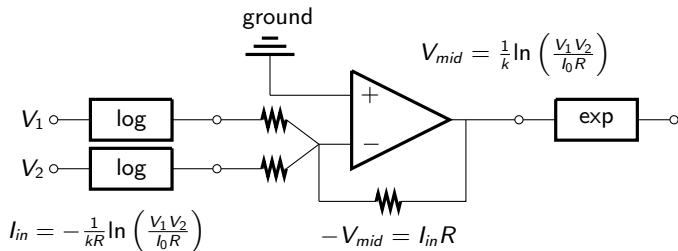

Multiplication operator

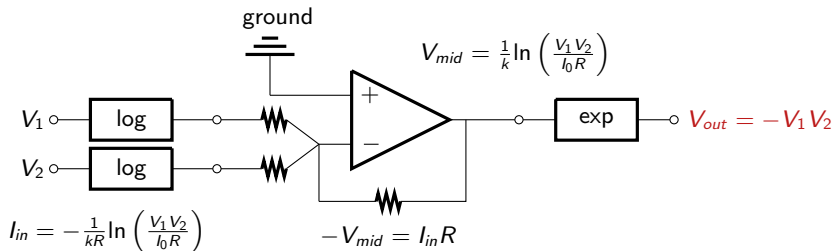

From Amplifier to Information Revolution

As amplifiers have developed from vacuum tube → transistor → integrated circuit embedded amplifier, combined with switching logic circuit, became modern processor which enable the Information Revolution

From Amplifier to Information Revolution

As amplifiers have developed from vacuum tube → transistor → integrated circuit embedded amplifier, combined with switching logic circuit, became modern processor which enable the Information Revolution

